
Signal Relay Analysis


August 2023

Schematic

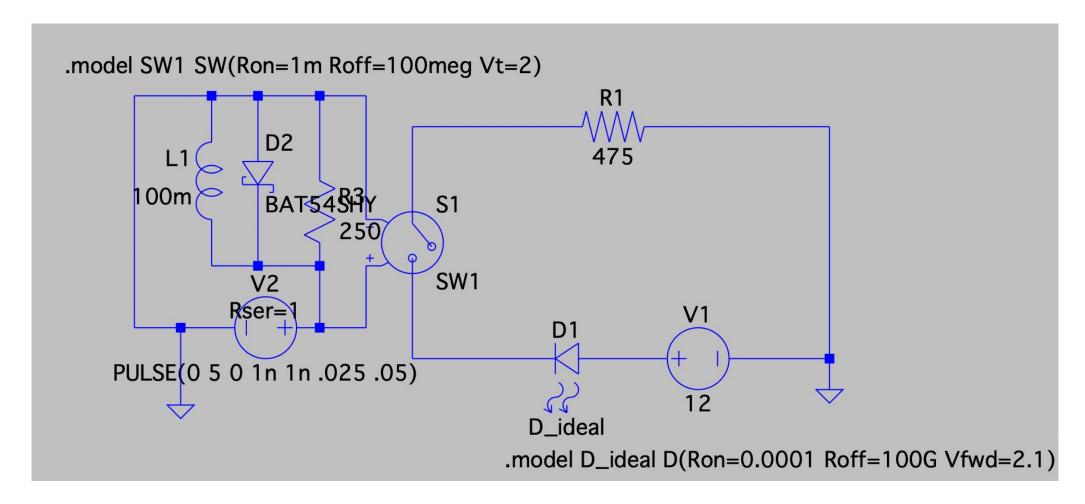


Since LTSpice doesn't have an existing model for this relay, I use R3 as the relay's resistance, L1 as the coil inside the relay, and S1 as the switch of the relay.


D2 (Flyback Diode in Primary Circuit)

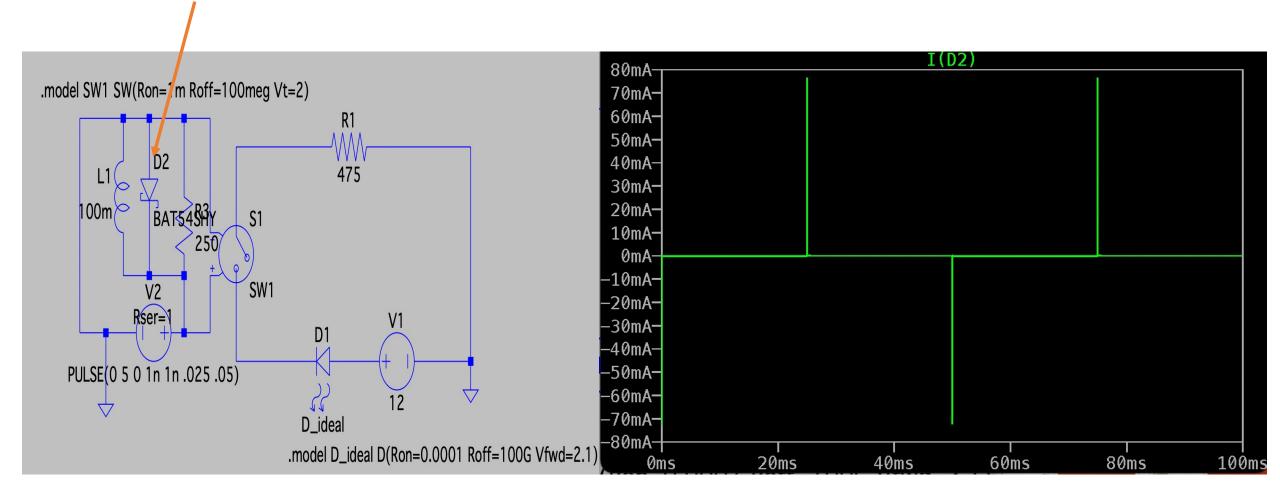


The flyback diode is used to protect the primary circuit when the voltage changes suddenly.

V2 (Power Supply in Primary Circuit)

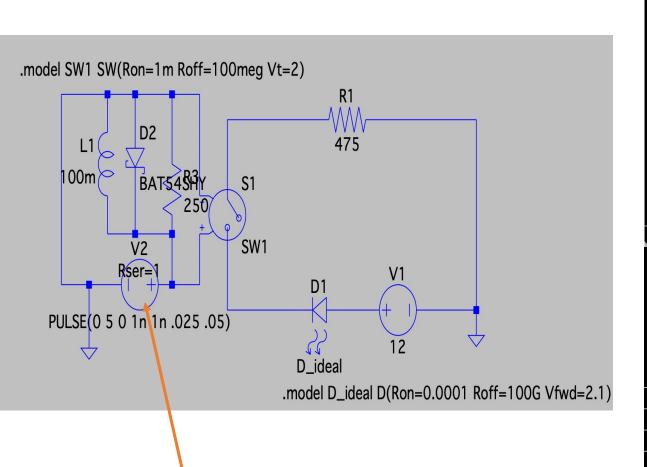


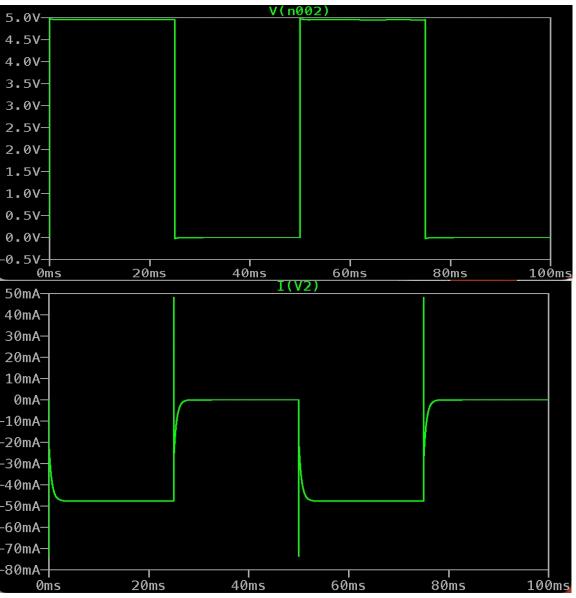


R3 (Resistance of Relay)

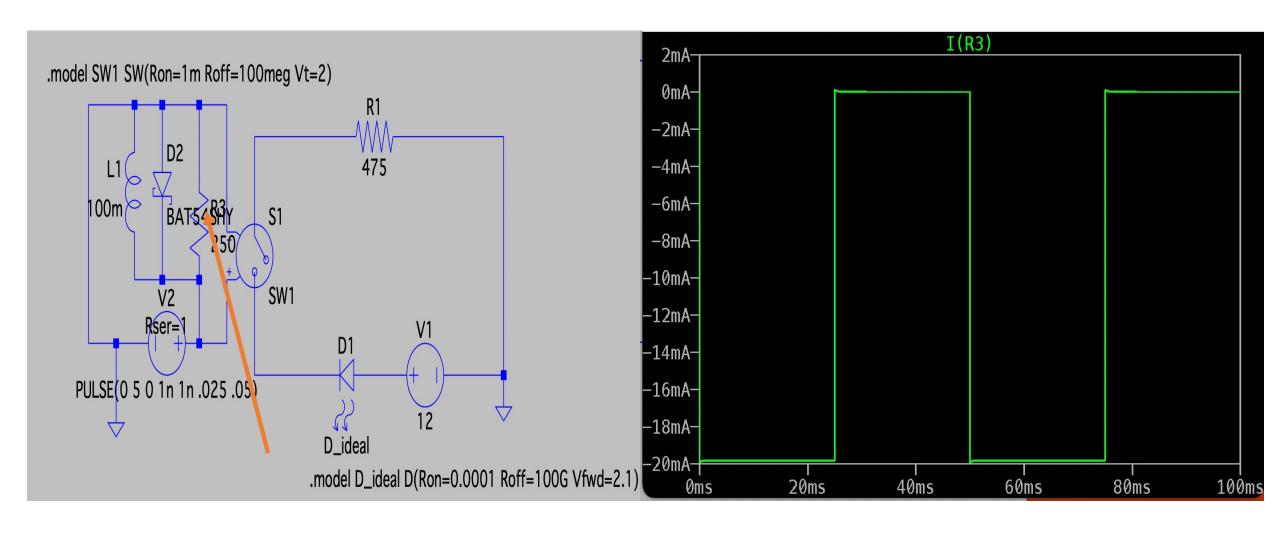

L1 (Coil inside Relay)

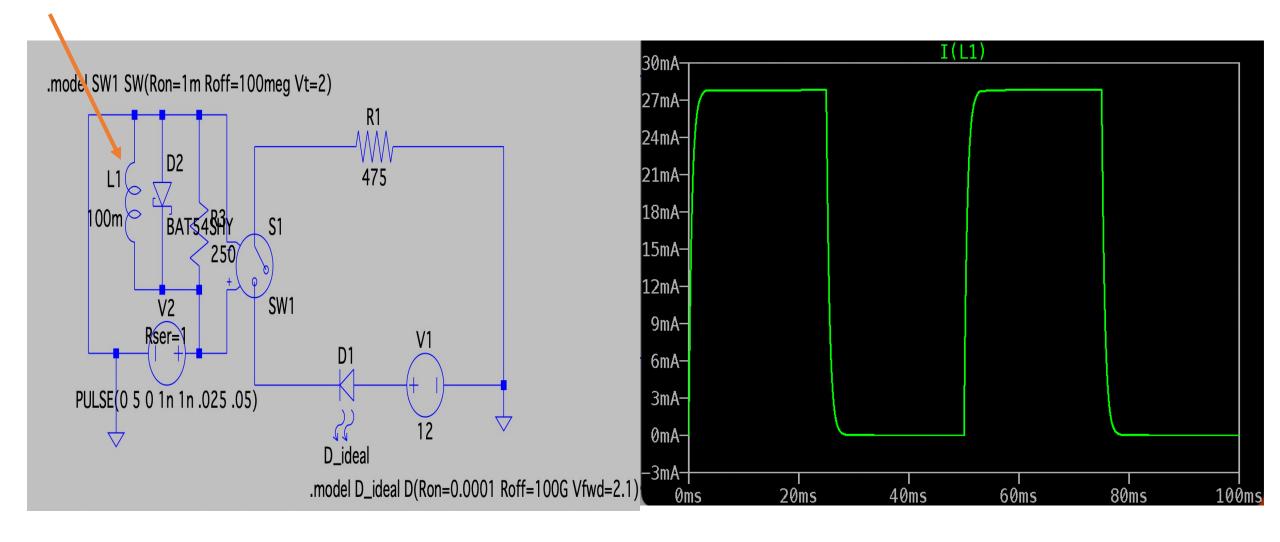


D1 (LED Light in Secondary Circuit)

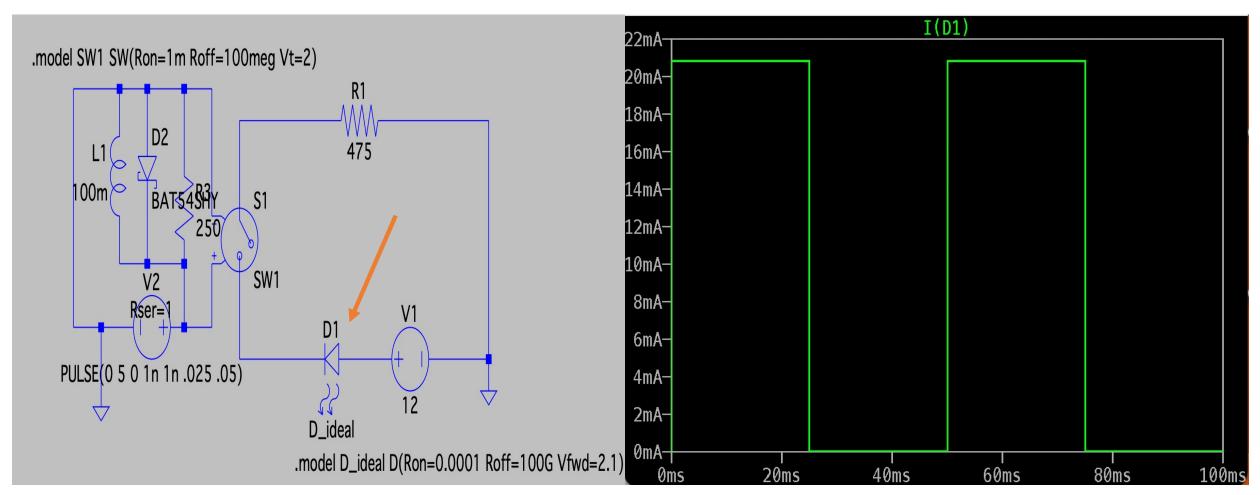


The light is used to check whether current appears in the secondary circuit.

R1 (Resistor in Secondary Circuit)

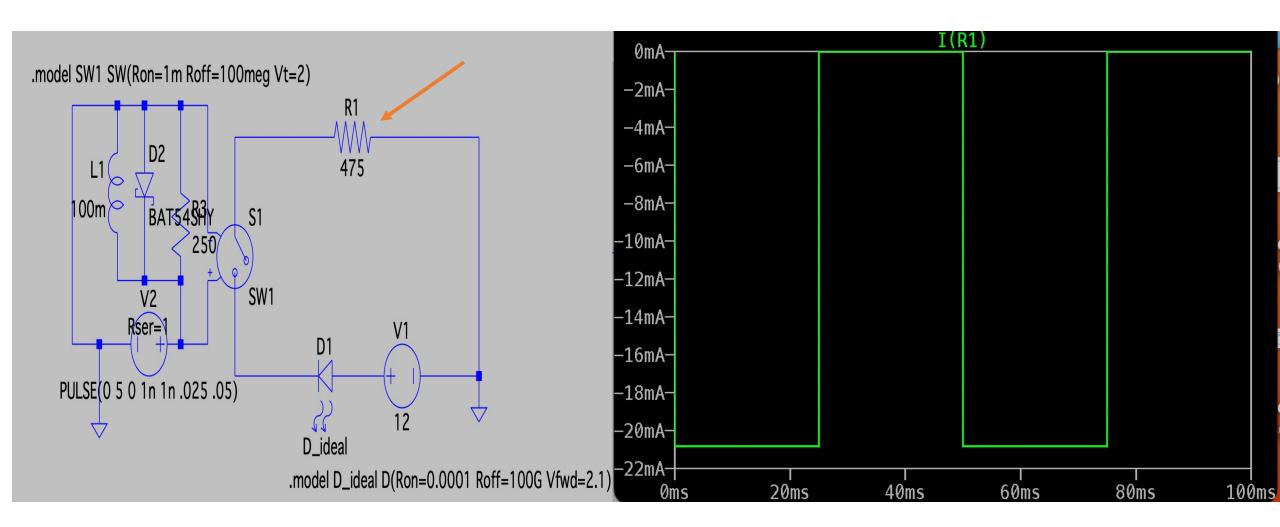


The resistor is used to protect secondary circuit.


V1 (Power Supply of Secondary Circuit)

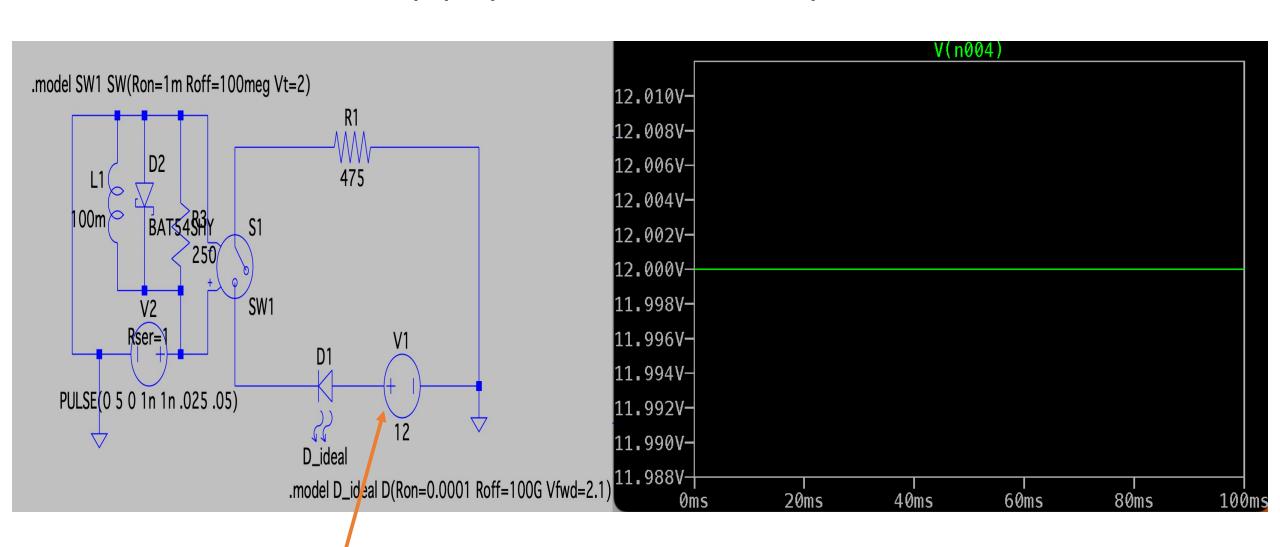

Voltage near LED Light

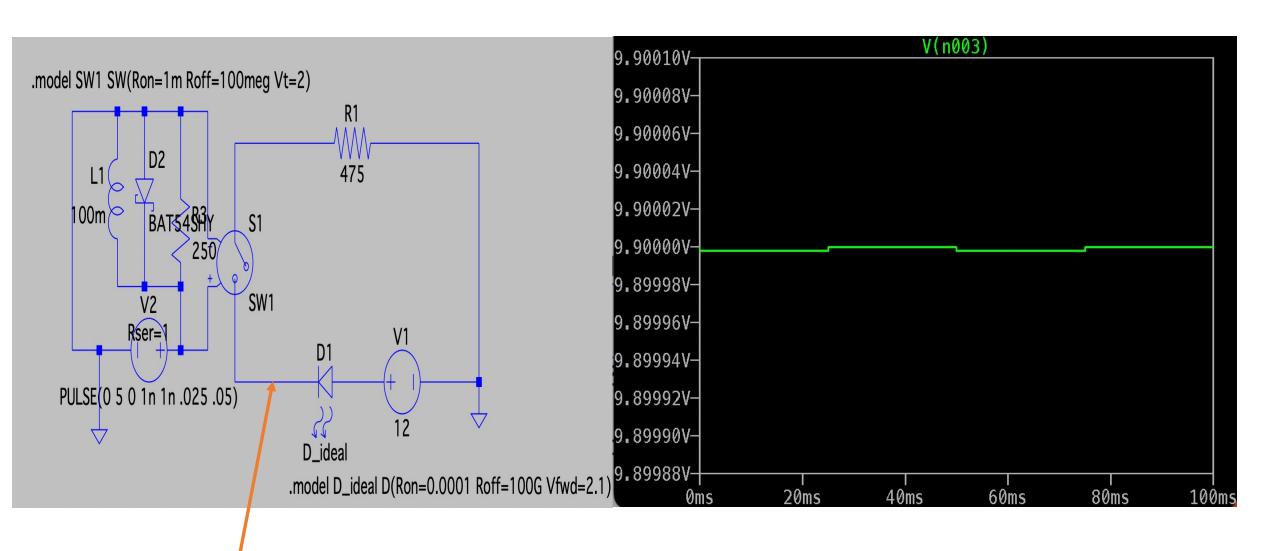

Voltage near Resistor

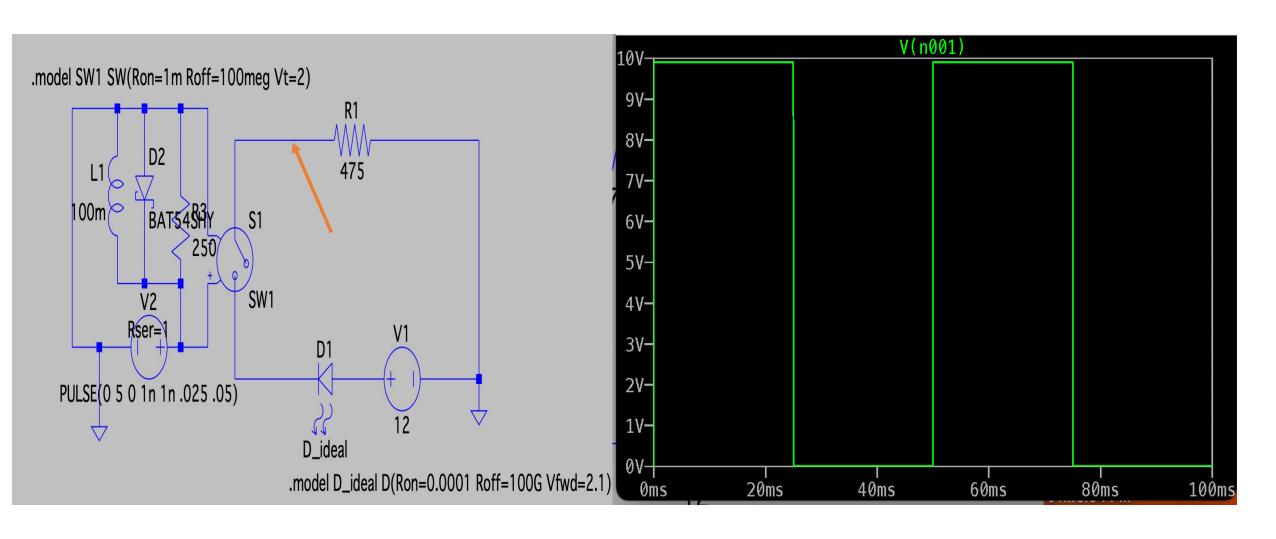

BOM (Bill of Material)

Qty	Description	Long Description	ROHS
1 (3)	Relay, Telecom, DPDT 2A 5VDC	Telecom Relay DPDT (2 Form C) Surface Mount	10
1 (0.27)	LED Red Clear 5mm round T/H	Red 624 nm LED Indication - Discrete 2.1V Radial	10
1 (0.3)	Res 475 ohm 0.4W 1% AXIAL	475 Ohms +-1% 0.4W Through Hole Resistor Axial Metal Film	10
1 (2.31)	Switch Pushbutton SPST 1A 30V	Pushbutton Switch SPST Standard Through Hole	3
1 (0.34)	Diode Schottky 40V 1A DO41	Diode 40V 1A Through Hole DO-41	10
1 (0.48)	Diode Schottky 30V 200MA DO35	Diode 30V 200mA Through Hole DO-35 (DO-204AH)	10
1 (0.40)	Diode Schottky 30 v 2001vin DO33	Diode 30 v 200 mA miodgii note Do-33 (Do-204An)	